

Exam

Name\_\_\_\_\_

TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.

- 1) A LOW input to an inverter produces a HIGH output.

1) \_\_\_\_\_

Answer: ☒ True      ☐ False
- 2) The OR gate performs a function similar to series-connected switches.

2) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 3) The output of an AND gate is HIGH only when all inputs are HIGH.

3) \_\_\_\_\_

Answer: ☒ True      ☐ False
- 4) The output of an AND gate is LOW only when all inputs are LOW.

4) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 5) When the inputs to a 3-input AND gate are 001, the output is HIGH.

5) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 6) When the inputs to a 3-input OR gate are 001, the output is HIGH.

6) \_\_\_\_\_

Answer: ☒ True      ☐ False
- 7) The output of an OR gate is HIGH when at least one input is HIGH.

7) \_\_\_\_\_

Answer: ☒ True      ☐ False
- 8) The output of an OR gate is LOW when at least one input is LOW.

8) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 9) The output of a NAND gate is HIGH only when one or more inputs are HIGH.

9) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 10) The output of a NAND gate is LOW only when all inputs are HIGH.

10) \_\_\_\_\_

Answer: ☒ True      ☐ False
- 11) The output of a NOR gate is LOW only when all inputs are HIGH.

11) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 12) The output of a NOR gate is HIGH only when all inputs are HIGH.

12) \_\_\_\_\_

Answer:    ☐ True      ☒ False
- 13) When the inputs to a 3-input NAND gate are 001, the output is HIGH.

13) \_\_\_\_\_

Answer: ☒ True      ☐ False
- 14) When the inputs to a 3-input NOR gate are 001, the output is LOW.


14) \_\_\_\_\_

Answer: ☒ True      ☐ False

- 15) The output of a 2-input Exclusive-OR gate is HIGH when the inputs are equal, or identical. 15) \_\_\_\_\_  
 Answer: True ☒ False
- 16) The output of a 2-input Exclusive-NOR gate is HIGH when the inputs are equal, or identical. 16) \_\_\_\_\_  
 Answer: ☒ True False
- 17) A circle, or "bubble," on a distinctive-shape logic symbol indicates a logic inversion. 17) \_\_\_\_\_  
 Answer: ☒ True False

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

 
- 18) The symbol below represents a(n) \_\_\_\_\_. 18) \_\_\_\_\_



- A) NAND gate  
 B) AND gate  
 C) OR gate  
 D) none of the above

Answer: B

 
- 19) The symbol below represents a(n) \_\_\_\_\_. 19) \_\_\_\_\_



- A) NAND gate  
 B) AND gate  
 C) OR gate  
 D) none of the above

Answer: B

 
- 20) The symbol below represents a(n) \_\_\_\_\_. 20) \_\_\_\_\_



- A) AND gate  
 B) Inverter  
 C) OR gate  
 D) none of the above

Answer: C

 - 21) The symbol below represents a(n) \_\_\_\_\_. 21) \_\_\_\_\_




- A) Inverter  
 B) OR gate  
 C) AND gate  
 D) none of the above

Answer: B

22) The symbol below represents a(n) \_\_\_\_\_.


22) \_\_\_\_\_

 

- A) OR gate
- B) Inverter
- C) AND gate
- D) NAND gate
- Answer: D

23) The symbol below represents a(n) \_\_\_\_\_.


23) \_\_\_\_\_

 

- A) Exclusive-NOR gate
- B) inverter
- C) NOR gate
- D) NAND gate
- Answer: C

24) The symbol below represents a(n) \_\_\_\_\_.


24) \_\_\_\_\_

 

- A) NOR gate
- B) NAND gate
- C) inverter
- D) Exclusive-NOR gate
- Answer: B

25) The symbol below represents a(n) \_\_\_\_\_.


25) \_\_\_\_\_

 

- A) AND gate
- B) NAND gate
- C) NOR gate
- D) OR gate
- Answer: C

26) The symbol below represents a(n) \_\_\_\_\_.


26) \_\_\_\_\_

 

- A) OR gate
- B) Exclusive-OR gate
- C) NAND gate
- D) AND gate
- Answer: B

27) The symbol below represents a(n) \_\_\_\_\_.

27) \_\_\_\_\_

 


- A) Exclusive-NOR gate
- B) Exclusive-OR gate
- C) NAND gate
- D) NOR gate

Answer: A

28) The symbol below represents a(n) \_\_\_\_\_.

28) \_\_\_\_\_

 

- A) Inverter
- B) OR gate
- C) AND gate
- D) NAND gate

Answer: A

29) The truth table below describes a(n) \_\_\_\_\_.

29) \_\_\_\_\_

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

- A) AND gate
- B) OR gate
- C) NOR gate
- D) NAND gate

Answer: A

30) The truth table below describes a(n) \_\_\_\_\_.

30) \_\_\_\_\_

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

- A) AND gate
- B) OR gate
- C) NOR gate
- D) NAND gate

Answer: B

31) The truth table below describes a(n) \_\_\_\_\_.

31) \_\_\_\_\_

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

- A) AND gate
- B) OR gate
- C) NOR gate
- D) NAND gate

Answer: D

32) The truth table below describes a(n) \_\_\_\_\_. 32) \_\_\_\_\_

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

- A) AND gate                      B) OR gate                      C) NOR gate                      D) NAND gate

Answer: C

33) Which of the truth tables below describes the Exclusive-NOR gate? 33) \_\_\_\_\_

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

- (A)                      (B)                      (C)                      (D)
- A) (A)                      B) (B)                      C) (C)                      D) (D)

Answer: A

 
34) The timing diagram below is correct for a 2-input \_\_\_\_\_ gate. 34) \_\_\_\_\_



- A) AND                      B) OR                      C) NAND                      D) Exclusive-OR

Answer: A

 
35) The timing diagram below is correct for a 2-input \_\_\_\_\_ gate. 35) \_\_\_\_\_



- A) AND                      B) OR                      C) NAND                      D) Exclusive-OR

Answer: C

 
36) The timing diagram below is correct for a 2-input \_\_\_\_\_ gate. 36) \_\_\_\_\_



- A) AND                      B) OR                      C) NAND                      D) Exclusive-OR

Answer: B

 
37) The timing diagram below is correct for a 2-input \_\_\_\_\_ gate. 37) \_\_\_\_\_



- A) AND                      B) OR                      C) Exclusive-NOR                      D) NOR

Answer: D

 
38) The timing diagram below is correct for a 2-input \_\_\_\_\_ gate. 38) \_\_\_\_\_



- A) NAND                      B) Exclusive-NOR                      C) AND                      D) Exclusive-OR

Answer: D

 39) The timing diagram below is correct for a 2-input \_\_\_\_\_ gate. 39) \_\_\_\_\_



- A) Exclusive-OR                      B) NAND                      C) AND                      D) Exclusive-NOR

Answer: D

40) IC's with a \_\_\_\_\_ prefix have a broad operating temperature range and are generally used by the military. 40) \_\_\_\_\_

- A) 74                      B) TTL                      C) 2N                      D) 54

Answer: D

- 41) The \_\_\_\_\_ series of IC's are pin, function and voltage-level compatible with the 74 series IC's. 41) \_\_\_\_\_  
 A) ALS B) 2N C) HCT D) CMOS  
 Answer: C
- 42) A logic gate draws 10mA when its output is HIGH and 20mA when its output is LOW. When operating from a 12V supply with a 10% duty cycle the average power dissipation will be \_\_\_\_\_. 42) \_\_\_\_\_  
 A) 228mW B) 360mW C) 324mW D) 180mW  
 Answer: A
- 43) The fanout for standard bipolar logic devices is \_\_\_\_\_. 43) \_\_\_\_\_  
 A) 5 B) 10 C) 2 D) 1  
 Answer: B
- 44) The term "hex inverter" refers to \_\_\_\_\_. 44) \_\_\_\_\_  
 A) six inverters in a single package B) an inverter which has six inputs  
 C) an inverter that has a history of failure D) a six-input symbolic logic device  
 Answer: A
- 45) Which type of gate can be used to add two bits? 45) \_\_\_\_\_  
 A) XNAND B) NOR C) NAND D) XOR  
 Answer: D
- 46) An AND gate is checked for operation and the following readings are taken on the gate: input A = 0.2 V, input B = 4.5 V, input C = 0.4 V, output = 4.9 V. What might be wrong with the gate? 46) \_\_\_\_\_  
 A) Input C is too high. B) The output is stuck high; the chip is bad.  
 C) The output is too low: it should be 5 V. D) Nothing is wrong with the gate.  
 Answer: B
- 47) When an open occurs on the input to a bipolar logic device, the output will \_\_\_\_\_. 47) \_\_\_\_\_  
 A) go LOW, because there is no current in an open circuit  
 B) go HIGH, since full voltage appears across an open  
 C) react to the open input as if it were a HIGH input  
 D) still be good, if only the good inputs are used  
 Answer: C
- 48) When an open occurs on the input of a CMOS gate, the output will \_\_\_\_\_. 48) \_\_\_\_\_  
 A) go LOW, because there is no current in an open circuit  
 B) go HIGH, since full voltage appears across an open  
 C) be treated as if the open input were a HIGH  
 D) be unpredictable; it may go HIGH or LOW  
 Answer: D
- 49) What technology allows a GAL to be reprogrammed again and again? 49) \_\_\_\_\_  
 A) TTL B) CMOS C) E2CMOS D) NMOS  
 Answer: C

50) What programmable arrays are in PLD's? 50) \_\_\_\_\_  
A) OR arrays and AND arrays B) OR arrays only  
C) AND arrays only D) NOR arrays

Answer: A

51) Which of the following is not a type of SPLD? 51) \_\_\_\_\_  
A) GAL B) RAM C) PLA D) PROM

Answer: B

52) The difference between a PLA and a PAL is \_\_\_\_\_. 52) \_\_\_\_\_  
A) the PAL has more possible product terms than the PLA  
B) the PLA has a programmable OR plane and a programmable AND plane while the PAL only has a programmable AND plane  
C) the PAL has a programmable OR plane and a programmable AND plane while the PLA only has a programmable AND plane  
D) PALs and PLAs are the same thing.

Answer: B

53) HDL stands for \_\_\_\_\_. 53) \_\_\_\_\_  
A) hardwire descriptive logic B) hardware description language  
C) hardwired digital logic D) none of the above

Answer: B

54) HDLs differ from \_\_\_\_\_ in that they include ways of describing propagation times and other logic characteristics. 54) \_\_\_\_\_  
A) software programming languages B) software digital logic  
C) software description languages D) none of the above

Answer: C

55) The \_\_\_\_\_ in a VHDL program defines the logic element and its inputs/outputs or ports. 55) \_\_\_\_\_  
A) source B) hardware C) entity D) architecture

Answer: C

56) The \_\_\_\_\_ in a VHDL program describes its logic operation. 56) \_\_\_\_\_  
A) source B) architecture C) entity D) hardware

Answer: B

57) A \_\_\_\_\_ IC comes with logic functions that are not programmed in and cannot be altered. 57) \_\_\_\_\_  
A) VHDL B) HDL C) fixed-function D) microcontroller

Answer: C