

## CHAPTER 3

### OHM'S LAW, ENERGY, AND POWER

#### BASIC PROBLEMS

##### SECTION 3-1 Ohm's Law

- $I$  is directly proportional to  $V$  and will change the same percentage as  $V$ .
  - $I = 3(1 \text{ A}) = \mathbf{3 \text{ A}}$
  - $I = 1 \text{ A} - (0.8)(1 \text{ A}) = 1 \text{ A} - 0.8 \text{ A} = \mathbf{0.2 \text{ A}}$
  - $I = 1 \text{ A} + (0.5)(1 \text{ A}) = 1 \text{ A} + 0.5 \text{ A} = \mathbf{1.5 \text{ A}}$
- When the resistance doubles, the current is halved from 100 mA to **50 mA**.
  - When the resistance is reduced by 30%, the current increases from 100 mA to  
 $I = V/0.7R = 1.429(V/R) = (1.429)(100 \text{ mA}) \cong \mathbf{143 \text{ mA}}$
  - When the resistance is quadrupled, the current decreases from 100 mA to **25 mA**.
- Tripling the voltage triples the current from 10 mA to 30 mA, but doubling the resistance halves the current to **15 mA**.

##### SECTION 3-2 Application of Ohm's Law

- $I = \frac{V}{R} = \frac{5 \text{ V}}{1 \Omega} = \mathbf{5 \text{ A}}$
  - $I = \frac{V}{R} = \frac{15 \text{ V}}{10 \Omega} = \mathbf{1.5 \text{ A}}$
  - $I = \frac{V}{R} = \frac{50 \text{ V}}{100 \Omega} = \mathbf{0.5 \text{ A}}$
  - $I = \frac{V}{R} = \frac{30 \text{ V}}{15 \text{ k}\Omega} = \mathbf{2 \text{ mA}}$
  - $I = \frac{V}{R} = \frac{250 \text{ V}}{4.7 \text{ M}\Omega} = \mathbf{53.2 \mu\text{A}}$
- $I = \frac{V}{R} = \frac{9 \text{ V}}{2.7 \text{ k}\Omega} = \mathbf{3.33 \text{ mA}}$
  - $I = \frac{V}{R} = \frac{5.5 \text{ V}}{10 \text{ k}\Omega} = \mathbf{550 \mu\text{A}}$
  - $I = \frac{V}{R} = \frac{40 \text{ V}}{68 \text{ k}\Omega} = \mathbf{588 \mu\text{A}}$
  - $I = \frac{V}{R} = \frac{1 \text{ kV}}{2 \text{ k}\Omega} = \mathbf{500 \text{ mA}}$
  - $I = \frac{V}{R} = \frac{66 \text{ kV}}{10 \text{ M}\Omega} = \mathbf{6.60 \text{ mA}}$
- $I = \frac{V}{R} = \frac{12 \text{ V}}{10 \Omega} = \mathbf{1.2 \text{ A}}$

7. (a)  $I = \frac{V}{R} = \frac{25 \text{ V}}{10 \text{ k}\Omega} = \mathbf{2.50 \text{ mA}}$  (b)  $I = \frac{V}{R} = \frac{5 \text{ V}}{2.2 \text{ M}\Omega} = \mathbf{2.27 \mu\text{A}}$
- (c)  $I = \frac{V}{R} = \frac{15 \text{ V}}{1.8 \text{ k}\Omega} = \mathbf{8.33 \text{ mA}}$
8. Orange, violet, yellow, gold, brown  $\equiv 37.4 \Omega \pm 1\%$
- $I = \frac{V_S}{R} = \frac{12 \text{ V}}{37.4 \Omega} = \mathbf{0.321 \text{ A}}$
9.  $I = \frac{24 \text{ V}}{37.4 \Omega} = 0.642 \text{ A}$
- 0.642 A is greater than 0.5 A, so **the fuse will blow.**
10. (a)  $V = IR = (2 \text{ A})(18 \Omega) = \mathbf{36 \text{ V}}$  (b)  $V = IR = (5 \text{ A})(47 \Omega) = \mathbf{235 \text{ V}}$
- (c)  $V = IR = (2.5 \text{ A})(620 \Omega) = \mathbf{1550 \text{ V}}$  (d)  $V = IR = (0.6 \text{ A})(47 \Omega) = \mathbf{28.2 \text{ V}}$
- (e)  $V = IR = (0.1 \text{ A})(470 \Omega) = \mathbf{47 \text{ V}}$
11. (a)  $V = IR = (1 \text{ mA})(10 \Omega) = \mathbf{10 \text{ mV}}$  (b)  $V = IR = (50 \text{ mA})(33 \Omega) = \mathbf{1.65 \text{ V}}$
- (c)  $V = IR = (3 \text{ A})(4.7 \text{ k}\Omega) = \mathbf{14.1 \text{ kV}}$  (d)  $V = IR = (1.6 \text{ mA})(2.2 \text{ k}\Omega) = \mathbf{3.52 \text{ V}}$
- (e)  $V = IR = (250 \mu\text{A})(1 \text{ k}\Omega) = \mathbf{250 \text{ mV}}$  (f)  $V = IR = (500 \text{ mA})(1.5 \text{ M}\Omega) = \mathbf{750 \text{ kV}}$
- (g)  $V = IR = (850 \mu\text{A})(10 \text{ M}\Omega) = \mathbf{8.5 \text{ kV}}$  (h)  $V = IR = (75 \mu\text{A})(47 \Omega) = \mathbf{3.53 \text{ mV}}$
12.  $V = IR = (3 \text{ A})(20 \text{ m}\Omega) = \mathbf{60 \text{ mV}}$
13. (a)  $V = IR = (3 \text{ mA})(27 \text{ k}\Omega) = \mathbf{81 \text{ V}}$  (b)  $V = IR = (5 \mu\text{A})(100 \text{ M}\Omega) = \mathbf{500 \text{ V}}$
- (c)  $V = IR = (2.5 \text{ A})(47 \Omega) = \mathbf{117.5 \text{ V}}$
14. (a)  $R = \frac{V}{I} = \frac{10 \text{ V}}{2 \text{ A}} = \mathbf{5 \Omega}$  (b)  $R = \frac{V}{I} = \frac{90 \text{ V}}{45 \text{ A}} = \mathbf{2 \Omega}$
- (c)  $R = \frac{V}{I} = \frac{50 \text{ V}}{5 \text{ A}} = \mathbf{10 \Omega}$  (d)  $R = \frac{V}{I} = \frac{5.5 \text{ V}}{10 \text{ A}} = \mathbf{0.55 \Omega}$
- (e)  $R = \frac{V}{I} = \frac{150 \text{ V}}{0.5 \text{ A}} = \mathbf{300 \Omega}$
15. (a)  $R = \frac{V}{I} = \frac{10 \text{ kV}}{5 \text{ A}} = \mathbf{2 \text{ k}\Omega}$  (b)  $R = \frac{V}{I} = \frac{7 \text{ V}}{2 \text{ mA}} = \mathbf{3.5 \text{ k}\Omega}$
- (c)  $R = \frac{V}{I} = \frac{500 \text{ V}}{250 \text{ mA}} = \mathbf{2 \text{ k}\Omega}$  (d)  $R = \frac{V}{I} = \frac{50 \text{ V}}{500 \mu\text{A}} = \mathbf{100 \text{ k}\Omega}$
- (e)  $R = \frac{V}{I} = \frac{1 \text{ kV}}{1 \text{ mA}} = \mathbf{1 \text{ M}\Omega}$

$$16. \quad R = \frac{V}{I} = \frac{6 \text{ V}}{2 \text{ mA}} = \mathbf{3 \text{ k}\Omega}$$

$$17. \quad (a) \quad R = \frac{V}{I} = \frac{8 \text{ V}}{2 \text{ A}} = \mathbf{4 \Omega}$$

$$(b) \quad R = \frac{V}{I} = \frac{12 \text{ V}}{4 \text{ mA}} = \mathbf{3 \text{ k}\Omega}$$

$$(c) \quad R = \frac{V}{I} = \frac{30 \text{ V}}{150 \mu\text{A}} = 0.2 \text{ M}\Omega = \mathbf{200 \text{ k}\Omega}$$

$$18. \quad I = \frac{V}{R} = \frac{3.2 \text{ V}}{3.9 \Omega} = \mathbf{0.82 \text{ A}}$$

### SECTION 3-3 Energy and Power

$$19. \quad P = \frac{W}{t} = \frac{26 \text{ J}}{10 \text{ s}} = \mathbf{2.6 \text{ W}}$$

$$20. \quad \text{Since } 1 \text{ watt} = 1 \text{ joule}, P = 350 \text{ J/s} = \mathbf{350 \text{ W}}$$

$$21. \quad P = \frac{W}{t} = \frac{7500 \text{ J}}{5 \text{ h}}$$

$$\left( \frac{7500 \text{ J}}{5 \text{ h}} \right) \left( \frac{1 \text{ h}}{3600 \text{ s}} \right) = \frac{7500 \text{ J}}{18,000 \text{ s}} = 0.417 \text{ J/s} = \mathbf{417 \text{ mW}}$$

$$22. \quad (a) \quad 1000 \text{ W} = 1 \times 10^3 \text{ W} = \mathbf{1 \text{ kW}}$$

$$(b) \quad 3750 \text{ W} = 3.750 \times 10^3 \text{ W} = \mathbf{3.75 \text{ kW}}$$

$$(c) \quad 160 \text{ W} = 0.160 \times 10^3 \text{ W} = \mathbf{0.160 \text{ kW}}$$

$$(d) \quad 50,000 \text{ W} = 50 \times 10^3 \text{ W} = \mathbf{50 \text{ kW}}$$

$$23. \quad (a) \quad 1,000,000 \text{ W} = 1 \times 10^6 \text{ W} = \mathbf{1 \text{ MW}}$$

$$(b) \quad 3 \times 10^6 \text{ W} = \mathbf{3 \text{ MW}}$$

$$(c) \quad 15 \times 10^7 \text{ W} = 150 \times 10^6 \text{ W} = \mathbf{150 \text{ MW}}$$

$$(d) \quad 8700 \text{ kW} = 8.7 \times 10^6 \text{ W} = \mathbf{8.7 \text{ MW}}$$

$$24. \quad (a) \quad 1 \text{ W} = 1000 \times 10^{-3} \text{ W} = \mathbf{1000 \text{ mW}}$$

$$(b) \quad 0.4 \text{ W} = 400 \times 10^{-3} \text{ W} = \mathbf{400 \text{ mW}}$$

$$(c) \quad 0.002 \text{ W} = 2 \times 10^{-3} \text{ W} = \mathbf{2 \text{ mW}}$$

$$(d) \quad 0.0125 \text{ W} = 12.5 \times 10^{-3} \text{ W} = \mathbf{12.5 \text{ mW}}$$

$$25. \quad (a) \quad 2 \text{ W} = \mathbf{2,000,000 \mu\text{W}}$$

$$(b) \quad 0.0005 \text{ W} = \mathbf{500 \mu\text{W}}$$

$$(c) \quad 0.25 \text{ mW} = \mathbf{250 \mu\text{W}}$$

$$(d) \quad 0.00667 \text{ mW} = \mathbf{6.67 \mu\text{W}}$$

$$26. \quad (a) \quad 1.5 \text{ kW} = 1.5 \times 10^3 \text{ W} = \mathbf{1500 \text{ W}}$$

$$(b) \quad 0.5 \text{ MW} = 0.5 \times 10^6 \text{ W} = \mathbf{500,000 \text{ W}}$$

$$(c) \quad 350 \text{ mW} = 350 \times 10^{-3} \text{ W} = \mathbf{0.350 \text{ W}}$$

$$(d) \quad 9000 \mu\text{W} = 9000 \times 10^{-6} \text{ W} = \mathbf{0.009 \text{ W}}$$

$$27. \quad P = \frac{W}{t} \text{ in watts}$$

$$V = \frac{W}{Q}$$

$$I = \frac{Q}{t}$$

$$P = VI = \frac{W}{t}$$

$$\text{So, } (1 \text{ V})(1 \text{ A}) = 1 \text{ W}$$

$$28. \quad P = \frac{W}{t} = \frac{1 \text{ J}}{1 \text{ s}} = 1 \text{ W}$$

$$1 \text{ kW} = 1000 \text{ W} = \frac{1000 \text{ J}}{1 \text{ s}}$$

$$1 \text{ kW-second} = 1000 \text{ J}$$

$$1 \text{ kWh} = 3600 \times 1000 \text{ J}$$

$$\mathbf{1 \text{ kWh} = 3.6 \times 10^6 \text{ J}}$$

### SECTION 3-4 Power in an Electric Circuit

$$29. \quad P = VI = (5.5 \text{ V})(3 \text{ mA}) = \mathbf{16.5 \text{ mW}}$$

$$30. \quad P = VI = (115 \text{ V})(3 \text{ A}) = \mathbf{345 \text{ W}}$$

$$31. \quad P = I^2 R = (500 \text{ mA})^2 (4.7 \text{ k}\Omega) = \mathbf{1.18 \text{ kW}}$$

$$32. \quad P = I^2 R = (5.0 \text{ A})^2 (20 \times 10^{-3} \Omega) = \mathbf{500 \text{ mW}}$$

$$33. \quad P = \frac{V^2}{R} = \frac{(60 \text{ V})^2}{620 \Omega} = \mathbf{5.81 \text{ W}}$$

$$34. \quad P = \frac{V^2}{R} = \frac{(1.5 \text{ V})^2}{56 \Omega} = 0.0402 \text{ W} = \mathbf{40.2 \text{ mW}}$$

$$35. \quad P = I^2 R$$

$$R = \frac{P}{I^2} = \frac{100 \text{ W}}{(2 \text{ A})^2} = \mathbf{25 \Omega}$$

36.  $5 \times 10^6 \text{ watts for 1 minute} = 5 \times 10^3 \text{ kWmin}$

$$\frac{5 \times 10^3 \text{ kWmin}}{60 \text{ min/1 hr}} = \mathbf{83.3 \text{ kWh}}$$

37.  $\frac{6700 \text{ W/s}}{(1000 \text{ W/kW})(3600 \text{ s/h})} = \mathbf{0.00186 \text{ kWh}}$

38.  $(50 \text{ W})(12 \text{ h}) = \mathbf{600 \text{ Wh}}$   
 $50 \text{ W} = 0.05 \text{ kW}$   
 $(0.05 \text{ kW})(12 \text{ h}) = \mathbf{0.6 \text{ kWh}}$

39.  $I = \frac{V}{R_L} = \frac{1.25 \text{ V}}{10 \Omega} = 0.125 \text{ A}$

$$P = VI = (1.25 \text{ V})(0.125 \text{ A}) = 0.156 \text{ W} = \mathbf{156 \text{ mW}}$$

40.  $P = \frac{W}{t}$   
 $156 \text{ mW} = \frac{156 \text{ mJ}}{1 \text{ s}}$   
 $W_{\text{tot}} = (156 \text{ mJ/s})(90 \text{ h})(3600 \text{ s/h}) = \mathbf{50,544 \text{ J}}$

### SECTION 3-5 The Power Rating of Resistors

41.  $P = I^2 R = (10 \text{ mA})^2 (6.8 \text{ k}\Omega) = 0.68 \text{ W}$   
 Use the next highest standard power rating of **1 W**.

42. If the 8 W resistor is used, it will be operating in a marginal condition.  
 To allow for a **safety margin of 20%**, use a **12 W** resistor.

### SECTION 3-6 Energy Conversion and Voltage Drop in a Resistance

43. (a) + at top, – at bottom of resistor      (b) + at bottom, – at top of resistor  
 (c) + on right, – on left of resistor

### SECTION 3-7 Power Supplies and Batteries

44.  $V_{\text{OUT}} = \sqrt{P_L R_L} = \sqrt{(1 \text{ W})(50 \Omega)} = \mathbf{7.07 \text{ V}}$

45. Ampere-hour rating =  $(1.5 \text{ A})(24 \text{ h}) = \mathbf{36 \text{ Ah}}$

$$46. \quad I = \frac{80 \text{ Ah}}{10 \text{ h}} = \mathbf{8 \text{ A}}$$

$$47. \quad I = \frac{650 \text{ mAh}}{48 \text{ h}} = \mathbf{13.5 \text{ mA}}$$

$$48. \quad P_{\text{LOST}} = P_{\text{IN}} - P_{\text{OUT}} = 500 \text{ mW} - 400 \text{ mW} = \mathbf{100 \text{ mW}}$$

$$\% \text{ efficiency} = \left( \frac{P_{\text{OUT}}}{P_{\text{IN}}} \right) 100\% = \left( \frac{400 \text{ mW}}{500 \text{ mW}} \right) 100\% = \mathbf{80\%}$$

$$49. \quad P_{\text{OUT}} = (\text{efficiency}) P_{\text{IN}} = (0.85)(5 \text{ W}) = \mathbf{4.25 \text{ W}}$$

## SECTION 3-8 Introduction to Troubleshooting

50. The 4th bulb from the left is open.

51. If should take **five** (maximum) resistance measurements.

## ADVANCED PROBLEMS

52. Assume that the total consumption of the power supply is the input power plus the power lost.

$$P_{\text{OUT}} = 2 \text{ W}$$

$$\% \text{ efficiency} = \left( \frac{P_{\text{OUT}}}{P_{\text{IN}}} \right) 100\%$$

$$P_{\text{IN}} = \left( \frac{P_{\text{OUT}}}{\% \text{ efficiency}} \right) 100\% = \left( \frac{2 \text{ W}}{60\%} \right) 100\% = 3.33 \text{ W}$$


The power supply itself uses

$$P_{\text{IN}} - P_{\text{OUT}} = 3.33 \text{ W} - 2 \text{ W} = 1.33 \text{ W}$$

$$\text{Energy} = W = Pt = (1.33 \text{ W})(24 \text{ h}) = 31.9 \text{ Wh} \cong \mathbf{0.032 \text{ kWh}}$$

$$53. \quad R_f = \frac{V}{I} = \frac{120 \text{ V}}{0.8 \text{ A}} = \mathbf{150 \Omega}$$

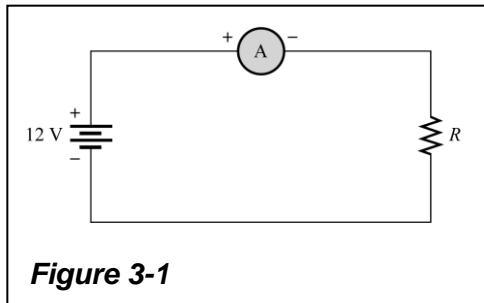54. Measure the current with an ammeter connected as shown in Figure 3-1. Then calculate the unknown resistance with the formula,  $R = 12 \text{ V}/I$ .



55. Calculate  $I$  for each value of  $V$ :

$$I_1 = \frac{0 \text{ V}}{100 \Omega} = 0 \text{ A} \qquad I_2 = \frac{10 \text{ V}}{100 \Omega} = 100 \text{ mA}$$


$$I_3 = \frac{20 \text{ V}}{100 \Omega} = 200 \text{ mA} \qquad I_4 = \frac{30 \text{ V}}{100 \Omega} = 300 \text{ mA}$$

$$I_5 = \frac{40 \text{ V}}{100 \Omega} = 400 \text{ mA} \qquad I_6 = \frac{50 \text{ V}}{100 \Omega} = 500 \text{ mA}$$

$$I_7 = \frac{60 \text{ V}}{100 \Omega} = 600 \text{ mA} \qquad I_8 = \frac{70 \text{ V}}{100 \Omega} = 700 \text{ mA}$$

$$I_9 = \frac{80 \text{ V}}{100 \Omega} = 800 \text{ mA} \qquad I_{10} = \frac{90 \text{ V}}{100 \Omega} = 900 \text{ mA}$$
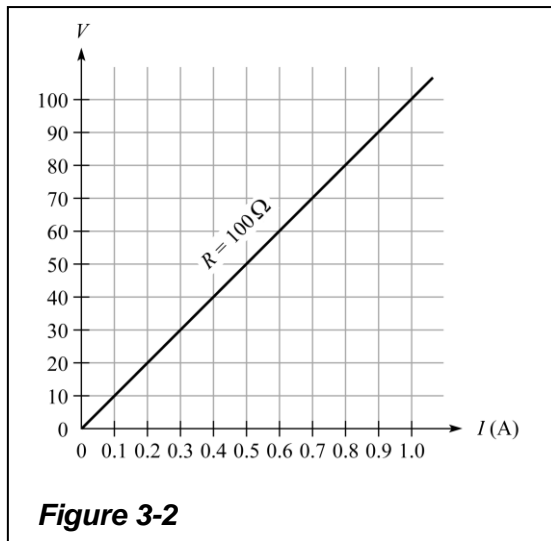
$$I_{11} = \frac{100 \text{ V}}{100 \Omega} = 1 \text{ A}$$



The graph is a straight line as shown in Figure 3-2. This indicates a *linear* relationship between  $I$  and  $V$ .

$$56. \quad R = \frac{V_s}{I} = \frac{1 \text{ V}}{5 \text{ mA}} = \mathbf{200 \, \Omega}$$

$$(a) \quad I = \frac{V_s}{R} = \frac{1.5 \text{ V}}{200 \, \Omega} = \mathbf{7.5 \text{ mA}}$$

$$(b) \quad I = \frac{V_s}{R} = \frac{2 \text{ V}}{200 \, \Omega} = \mathbf{10 \text{ mA}}$$

$$(c) \quad I = \frac{V_s}{R} = \frac{3 \text{ V}}{200 \, \Omega} = \mathbf{15 \text{ mA}}$$

$$(d) \quad I = \frac{V_s}{R} = \frac{4 \text{ V}}{200 \, \Omega} = \mathbf{20 \text{ mA}}$$

$$(e) \quad I = \frac{V_s}{R} = \frac{10 \text{ V}}{200 \, \Omega} = \mathbf{50 \text{ mA}}$$

$$57. \quad R_1 = \frac{V}{I} = \frac{1 \text{ V}}{2 \text{ A}} = \mathbf{0.5 \, \Omega} \quad R_2 = \frac{V}{I} = \frac{1 \text{ V}}{1 \text{ A}} = \mathbf{1 \, \Omega} \quad R_3 = \frac{V}{I} = \frac{1 \text{ V}}{0.5 \text{ A}} = \mathbf{2 \, \Omega}$$

$$58. \quad \frac{V_2}{30 \text{ mA}} = \frac{10 \text{ V}}{50 \text{ mA}}$$

$$V_2 = \frac{(10 \text{ V})(30 \text{ mA})}{50 \text{ mA}} = 6 \text{ V} \quad \mathbf{\text{new value}}$$

**The voltage decreased by 4 V, from 10 V to 6 V.**

59. The current increase is 50%, so the voltage increase must be the same; that is, the voltage must be increased by  $(0.5)(20 \text{ V}) = \mathbf{10 \text{ V}}$ .

The new value of voltage is  $V_2 = 20 \text{ V} + (0.5)(20 \text{ V}) = 20 \text{ V} + 10 \text{ V} = \mathbf{30 \text{ V}}$

$$60. \quad \text{Wire resistance: } R_w = \frac{(10.4 \text{ CM} \cdot \Omega/\text{ft})(24 \text{ ft})}{1624.3 \text{ CM}} = 0.154 \, \Omega$$

$$(a) \quad I = \frac{V}{R + R_w} = \frac{6 \text{ V}}{100.154 \, \Omega} = \mathbf{59.9 \text{ mA}}$$

$$(b) \quad V_R = (59.9 \text{ mA})(100 \, \Omega) = \mathbf{5.99 \text{ V}}$$

$$(c) \quad V_{R_w} = 6 \text{ V} - 5.99 \text{ V} = 0.01 \text{ V}$$

$$\text{For one length of wire, } V = \frac{0.01 \text{ V}}{2} = \mathbf{0.005 \text{ V}}$$

$$61. \quad 300 \text{ W} = 0.3 \text{ kW} \\ 30 \text{ days} = (30 \text{ days})(24 \text{ h/day}) = 720 \text{ h} \\ \text{Energy} = (0.3 \text{ kW})(720 \text{ h}) = \mathbf{216 \text{ kWh}}$$


$$62. \quad \frac{1500 \text{ kWh}}{31 \text{ days}} = 48.39 \text{ kWh/day} \\ P = \frac{48.39 \text{ kWh/day}}{24 \text{ h/day}} = \mathbf{2.02 \text{ kW}}$$



63. The minimum power rating you should use is **12 W** so that the power dissipation does not exceed the rating.
64. (a)  $P = \frac{V^2}{R} = \frac{(12\text{ V})^2}{10\ \Omega} = \mathbf{14.4\text{ W}}$   
 (b)  $W = Pt = (14.4\text{ W})(2\text{ min})(1/60\text{ h/min}) = \mathbf{0.48\text{ Wh}}$   
 (c) Neither, the power is the same because it is not time dependent.
65.  $V_{R(\text{max})} = 120\text{ V} - 100\text{ V} = 20\text{ V}$   
 $I_{\text{max}} = \frac{V_{R(\text{max})}}{R_{\text{min}}} = \frac{20\text{ V}}{8\ \Omega} = 2.5\text{ A}$   
 A fuse with a rating of less than 2.5 A must be used. **A 2 A fuse is recommended.**
66.  $I = \sqrt{\frac{P}{R}} = \sqrt{\frac{0.5\text{ W}}{0.030\ \Omega}} = \mathbf{4.08\text{ A}}$
67. Power will increase by four times.
66. The materials required for the Load Test Box are as follows:

Item	Component	Qty
1	Resistor: 5.0 $\Omega$ , 10 W	1
2	Resistor: 16 $\Omega$ , 5 W	1
3	Resistor: 100 $\Omega$ , 2.0 W	1
4	Resistor: 150 $\Omega$ , 3.0 W	1
5	1 pole, 4 position rotary switch	1
6	Knob	1
7	Enclosure (4" x 4" x 2" Al)	1
8	Banana plug terminals	2
9	Fuse (1.5 A) and fuse holder	1
10	PC board (etched with pattern)	1
11	Screws, washers, nuts	4
12	Standoffs	4

69. See Figure 3-3.

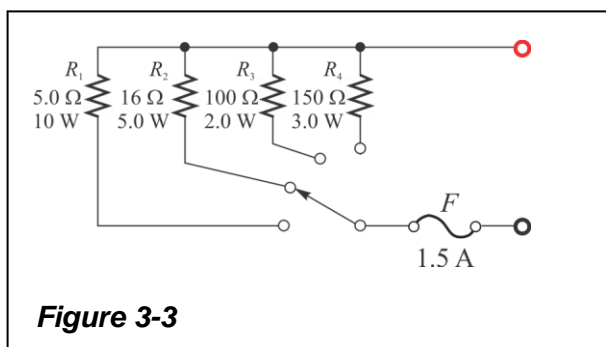

### Multisim Troubleshooting Problems

70.  $R$  is open.
71. No fault
72.  $R_1$  is shorted.
73. Lamp 4 is shorted.
74. Lamp 6 is open.